

Digital Logic Design



Hajar Falahati

Department of Computer Engineering
IRAN University of Science and Technology

hfalahati@iust.ac.ir

Circuit Logics

 
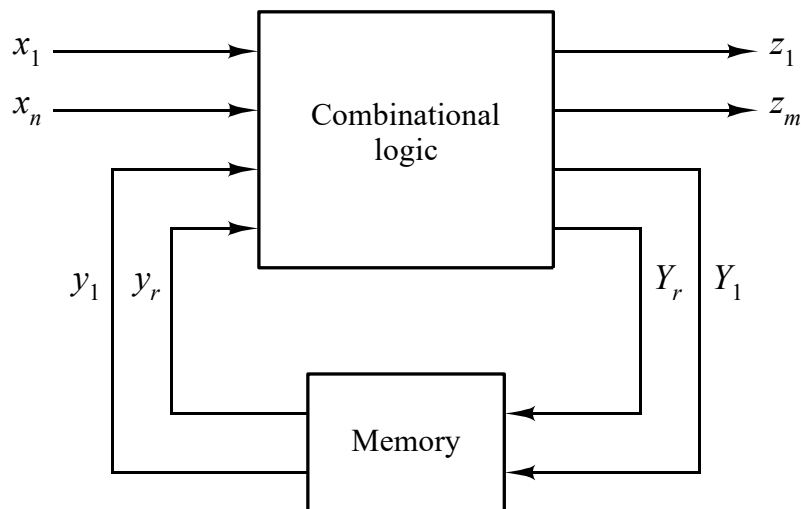
- Combinational logic
 - **Always inputs** produce the **output**
 - **Combinational logics** are **memory less**
 - **Memory-less circuits** **do not** contain any **feedback** lines
- Sequential logic
 - **Always inputs** and current state produce the **output**
 - They **have memory**
 - They **contain feedback lines**



Memory Unit

- An element which **stores one bit** data

- S-R latch
- S-R FF

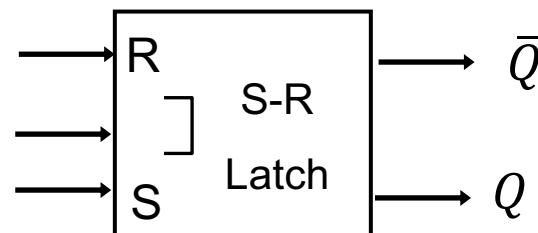 

Outline

- Memory devices
 - Flip Flops (FF)



Flip Flops

Delay Flip Flop (D-FF)

- Input

- D
- CLK

- Output


- Send D to the output

CLK	D	Q	$\bar{Q}$
0	X	Q	$\bar{Q}$
1	0	0	1
1	1	1	0


Hold the value

Send D to Q

Send D to Q

 


D-FF: Characteristics

 

Enable input C	Excitation input D	Present state Q	Next state Q^*
0	$\times$	0	0
0	$\cdot$	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

(a)

 


(b)


$$Q^* = DC + C'Q$$

D-FF: Implementation


- Using S-R FF

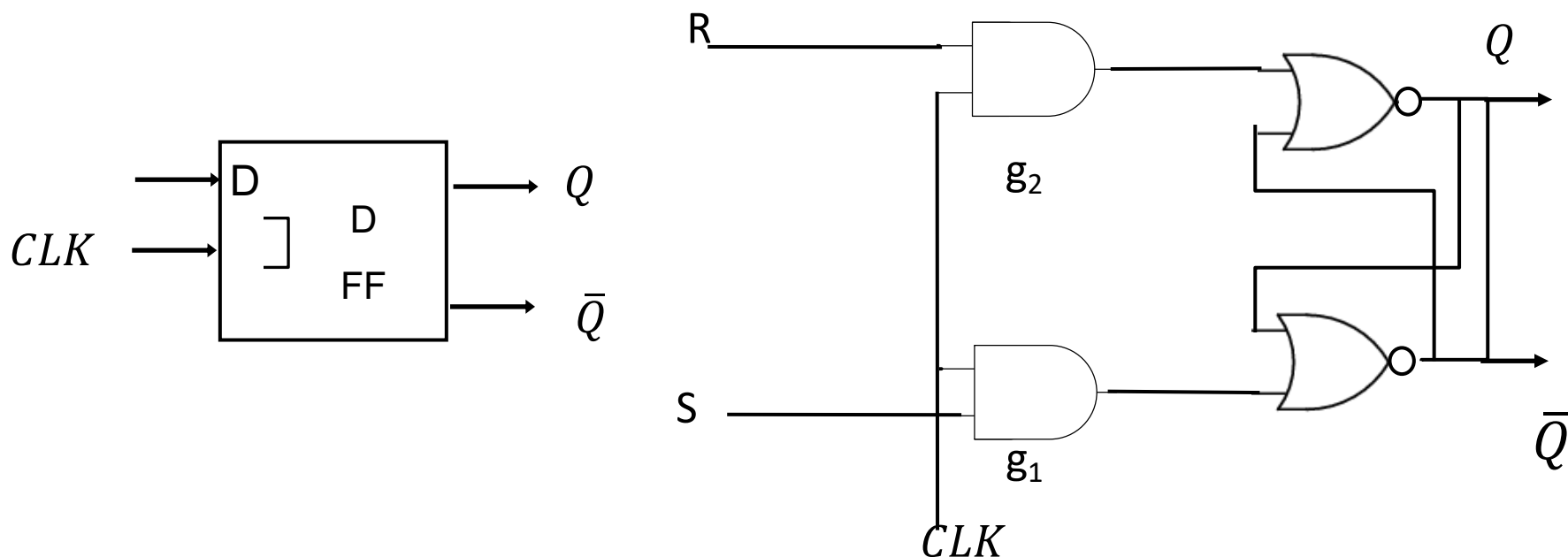


D-FF: Implementation (cont'd)

 

(a)

 


(b)




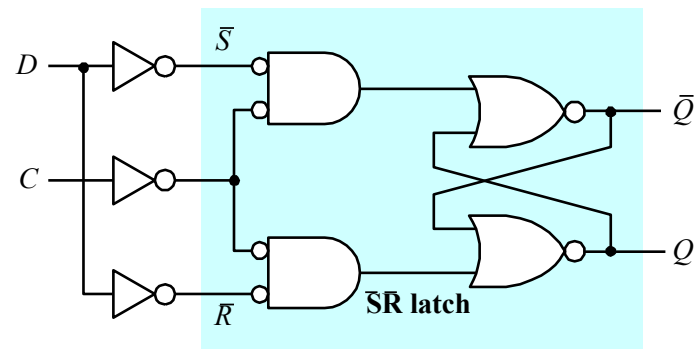


(c)

D-FF: Timing Diagram

 



D FF: Hazard-free

   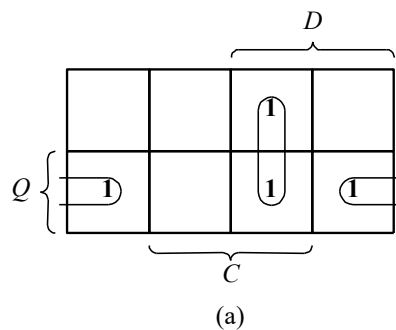

$$Q^* = DC + C'Q + DQ$$

Level-Triggered D-FF

  - CLK signal aim to manage changes in latches
- Inputs changes at different times




Edge-Triggered D-FF

- Output changes only at the positive or negative edge of CLK signal

POS & NEG Edge Triggered **D**


Positive Edge Trigger

 

D	CLK	Q	$\bar{Q}$
0	↑	0	1
1	↑	1	0

↑ : Rising Edge of Clock

Negative Edge Trigger


 


D	CLK	Q	$\bar{Q}$
0	↓	0	1
1	↓	1	0



↓ : Falling Edge of Clock

Edge-Triggered D-FF: Timing Analysis

- Determine Q

  


  Edge-Triggered D-FF: Timing Analysis (cont'd)





Edge-Triggered D-FF: Timing Analysis (cont'd)

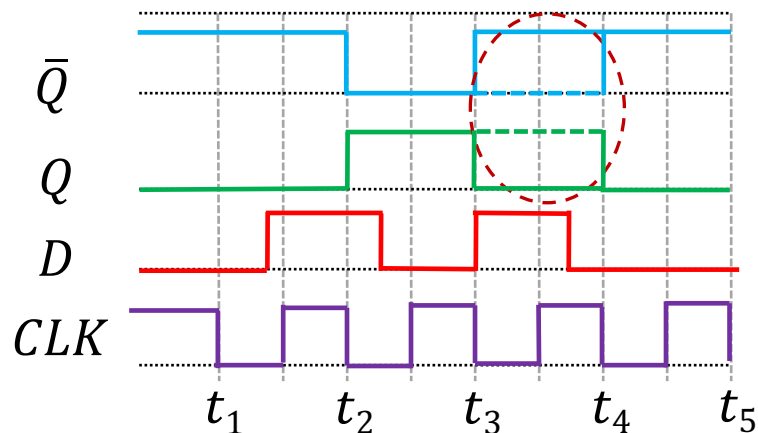- What happens at t_3 ?
 - There is a race between D and CLK
- D wins
 - FF becomes 1 (dashed lines)
- CLK wins
 - FF becomes 0




Critical Race

  - Overcome the critical race between CLK and input
 - Setup time (t_s)
 - Hold time (t_h)




Hold Time and Setup Time

 - Setup time (t_s)
 - **Minimum time interval**
 - **Before** the sampling event of the **clock**
 - Input signal must be **stable** (unchanging)
 - To be recognized correctly
- Hold time (t_h)
 - **Minimum time interval**
 - **After** the sampling event of the **clock**
 - Input signal must be **stable** (unchanging)
 - To be recognized correctly



D-FF: Timing Constraints

 

Reset

- Reset input

- Reset the FF value
- $Q = 0$
- A.k.a., clear (CLR)


- Types

- Synchronous

- Dependent to CLK signal
- Reset the value only when the CLK signal is active
 - Next clock edge arrives




- Asynchronous

 - Independent to CLK signal
- Reset the value only without considering the CLK signal state
- Quick but dangerous



R	C	D	Q	Q'
0	X	X	0	1
1	↑	0	0	1
1	↑	1	1	0


Reset (cont'd)

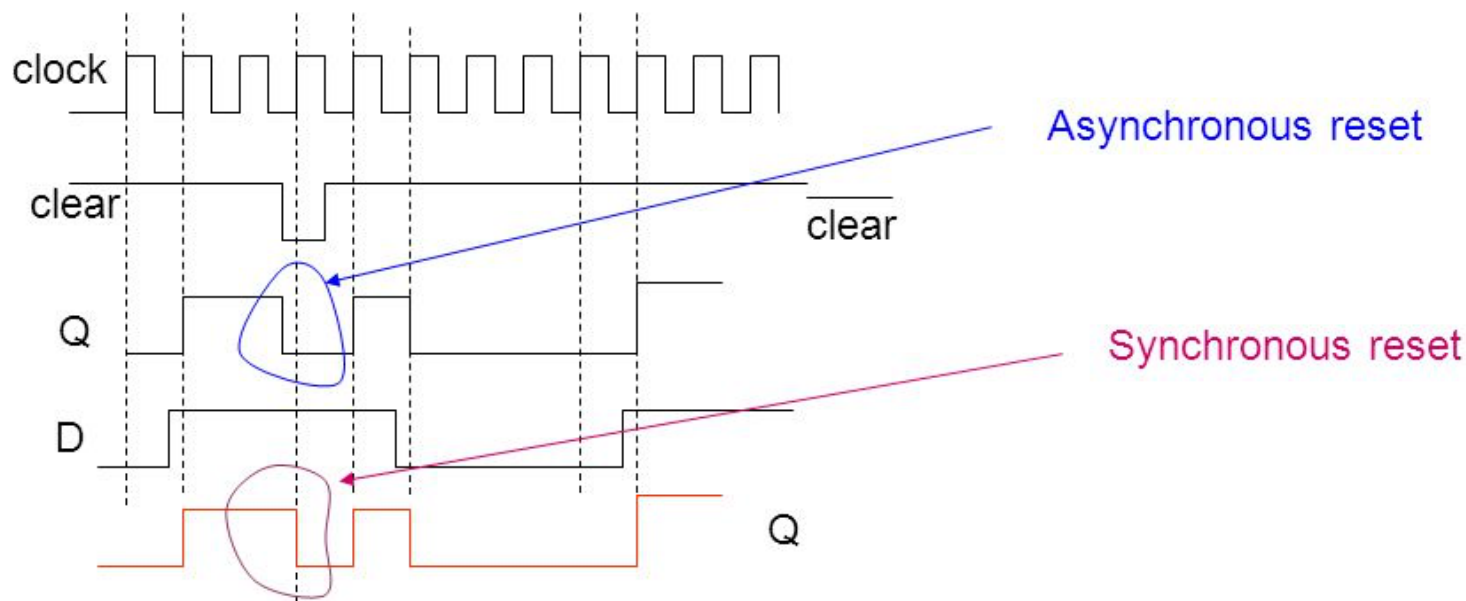  

Preset

- Preset input

 - Reset the FF value
- $Q = 1$
- A.k.a., PRE



- Types

- Synchronous
 - Dependent to CLK signal
- Asynchronous
 - Independent to CLK signal

Inputs				Outputs		Mode
$\overline{PRE}$	$\overline{CLR}$	D	CLK	Q	$\overline{Q}$	
L	H	x	x	H	L	Set
H	L	x	x	L	H	Clear
L	L	x	x	H	H	Not allowed
H	H	H	$\uparrow$	H	L	Clocked operation
H	H	L	$\uparrow$	L	H	Clocked operation
H	H	x	L	Q_0	$\overline{Q}_0$	Hold


JK Flip Flop (JK-FF)

- Input

- J
- K
- CLK

- Output

- 4 states

 

J	K	Q	C	Q^*
0	0	0		0 Hold
0	0	1		1
0	1	0		0 Reset
0	1	1		0
1	0	0		1 Set
1	0	1		1
1	1	0		1 Toggle
1	1	1		0


JK-FF: Characteristics

J	K	Q	C	Q^*
0	0	0		0 Hold
0	0	1		1
0	1	0		0 Reset
0	1	1		0
1	0	0		1 Set
1	0	1		1
1	1	0		1 Toggle
1	1	1		0

(a)



(b)


 


(c)

$$Q^* = K'Q + JQ'$$

JK-FF: Implementation

- Using D-FF

  


T Flip Flop (T-FF)

- **Input**

- T
- CLK

- **Output**

- Toggling
- 2 states

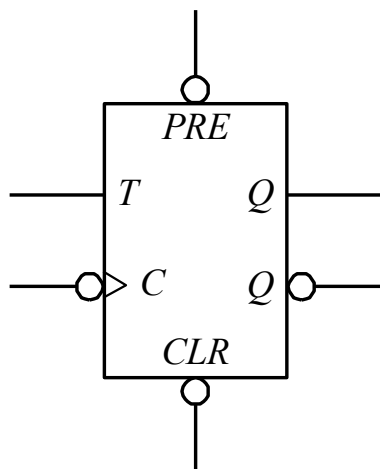

T	Q	C	Q^*
0	0	↓	0 Hold
0	1	↓	1
1	0	↓	1 Toggle
1	1	↓	0


$$Q^* = T'Q + TQ'$$

T-FF: Characteristics

T	Q	C	Q^*
0	0	↓	0
0	1	↓	1
1	0	↓	1
1	1	↓	0

Hold



Toggle

 

$$Q^* = T'Q + TQ'$$

T FF: Implementation



- Using JK FF

  

Master Slave


Edge-Triggered FF

  - How to implement an edge triggered flip flop?





Master-Slave SR FF



 
- One solution is using two level triggered flipflop



Master-Slave SR FF (cont'd)

  


Master-Slave SR FF (cont'd)

 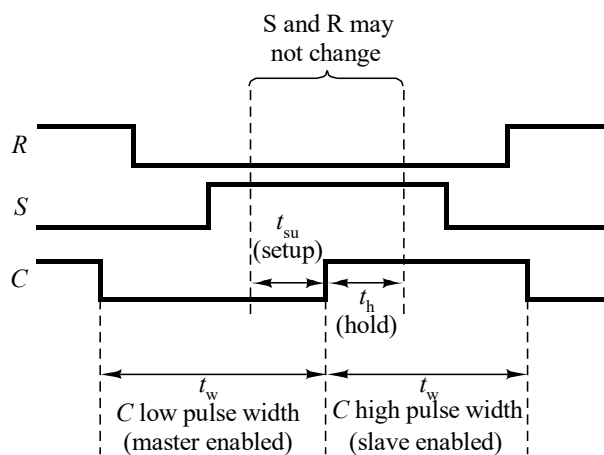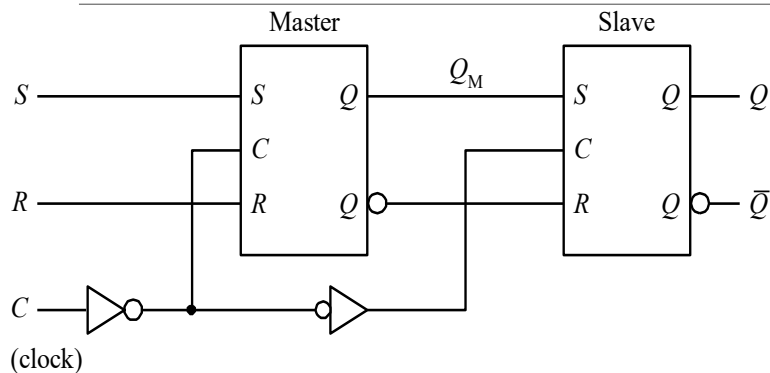

Flip-flop output can change


Master-Slave D Flip-flop

 - One solution is using two level triggered flipflop




Positive Edge Triggered D FF

 - Another solution is using three SR latches
 - **Two** latches respond to **inputs**
 - Data and CLK
 - **One** latch provides the **output**




Positive Edge Triggered D FF + Reset

- Asynchronous reset

 


Standard MSI D Latch

- 74LS75 quad D latch

 



Standard MSI D FF

- 74LS175 quad D FF

 


Standard MSI D FF (cont'd)

 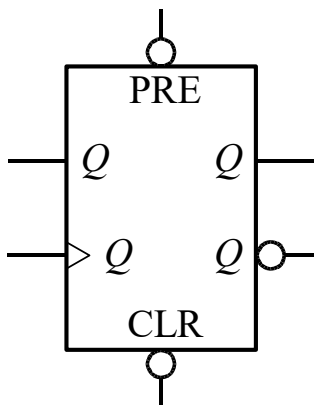- SN7474 dual positive-edge-triggered D Flip-Flop





Standard MSI JK FF

 - 74LS73A Dual Negative-edge-triggered JK FF



Standard MSI JK FF (cont'd)

  - SN7476 Dual Pulse-Triggered JK Flip-Flop



Thank You

